

**ADITYA UNIVERSITY**

B.Tech – I Semester End Examinations Regular – Dec 2024

BASIC ELECTRICAL AND ELECTRONICS ENGINEERING
(Common to CE, ME, ECE, CSE & Min.E)

Time: 3 hours

Max. Marks: 50


Answer ONE question from each unit

All Questions Carry Equal Marks

All parts of the questions must be answered at one place only

UNIT-I

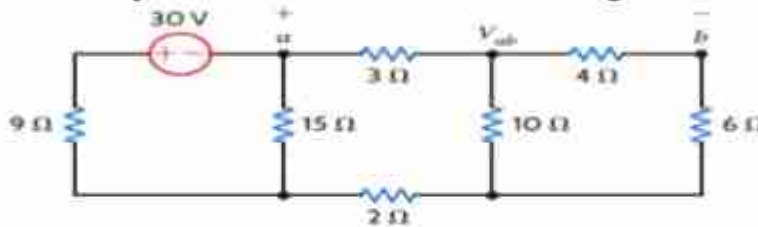- 1 a Define the following: i) Potential Difference ii) Resistance L2 CO1 [5M]
iii) Inductance iv) Capacitance v) Work
- b Using the KVL equations, find the V_{ab} in the following circuit. L3 CO1 [5M]



(OR)

- 2 a Derive an expression for the equivalent inductance when the inductances are connected in parallel. L3 CO1 [5M]
- b Derive an expression for the equivalent capacitance when the capacitances are connected in series. L3 CO1 [5M]

UNIT-II

- 3 a Explain the principle of operation of DC generator. L2 CO2 [5M]
- b Explain the working of repulsion type moving iron instrument. L2 CO2 [5M]

(OR)

- 4 a Describe the operation of a single phase transformer. L2 CO2 [5M]
- b Explain the operation of three phase induction motor. L2 CO2 [5M]

UNIT-III

- 5 a List and briefly explain any five conventional and five non-conventional energy resources. L2 CO3 [5M]
- b Explain the layout and operation of hydro power plant. L2 CO3 [5M]

(OR)

- 6 a Compare and contrast the advantages and disadvantages of solar power generation and wind power generation. L3 CO3 [5M]
- b Explain the working principle of a thermal power plant with a neat diagram. L3 CO3 [5M]

UNIT-IV

- 7 a Explain the impact of temperature variations on the conductivity of intrinsic and extrinsic semiconductors. L2 CO4 [5M]
- b Explain a simple common base configuration of BJT. L2 CO4 [5M]

(P.T.O)

(OR)

- 8 a Explain the input and output characteristics of a common emitter (CE) transistor configuration. L2 CO4 [5M]
b Explain the performance of a Zener diode as a voltage regulator. L5 CO4 [5M]

UNIT-V

- 9 a Analyze the ripple factor of a half-wave rectifier and full-wave rectifier. L4 CO5 [5M]
b Explain the working of universal gates (NAND and NOR) in digital logic design. L5 CO5 [5M]

(OR)

- 10 a Explain a simple DC power supply circuit using a full-wave bridge rectifier and a capacitor filter. Calculate the expected output voltage and ripple voltage for given input parameters. L2 CO5 [5M]
b Write the truth tables for NOT, OR, AND gates. L2 CO5 [5M]
