

H.T.No:

--	--	--	--	--	--	--	--	--	--

Course Code: 241EE001



ADITYA UNIVERSITY

B.Tech – I Semester End Examinations Supplementary – APR 2025

BASIC ELECTRICAL AND ELECTRONICS ENGINEERING (Common to CE, ME, ECE, CSE & Min.E)

Time: 3 hours

Max. Marks: 50

Answer ONE question from each unit

All Questions Carry Equal Marks

All parts of the questions must be answered at one place only

UNIT-I

- 1 a Define ohms law and write it's limitations L1 CO1 [5M]
b Calculate the resistance between the terminals P and Q of the network L3 CO1 [5M] shown in Fig.1.

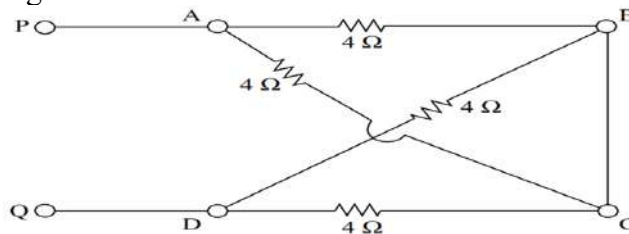


Fig.1

(OR)

- 2 a Derive the equation for Rms value, average value, peak factor and L3 CO1 [5M]
form factor for sinusoidal waveform
b Three resistances 100 ohm, 200 ohm and 300 ohm are connected in L3 CO1 [5M]
series to a 250 volt supply. Determine the current in the circuit and
the power dissipated in each resistor.

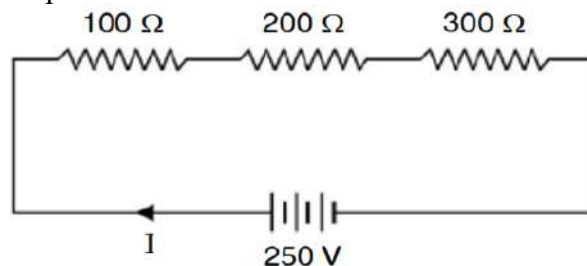


Fig.2

UNIT-II

- 3 a Explain the principle of operation of DC generator. L2 CO2 [5M]
b Explain the working of PMMC instrument with neat diagram L2 CO2 [5M]
(OR)
4 a Explain the operation of transformer with neat diagram . L2 CO2 [5M]
b Explain the working of Megger with neat diagram. L2 CO2 [5M]

(P.T.O)

UNIT-III

- 5 a Explain the schematic diagram of a Hydroelectric Power Plant. L2 CO3 [5M]
b Explain the process of earthing and describe its different types. L2 CO3 [5M]

(OR)

- 6 a Describe the working principle and layout of a solar power generation system. L2 CO3 [5M]
b A consumer uses a 10kW geyser, a 6kW electric furnace and five 100W bulbs for 15 hours. How many units (kWh) of electrical energy have been used and what would be the electricity bill? L3 CO3 [5M]

UNIT-IV

- 7 a Explain CB configuration of BJT L2 CO4 [5M]
b Draw and explain the input and output characteristics of a common-emitter configuration. L3 CO4 [5M]

(OR)

- 8 a Describe the operation of PNP transistor. L2 CO4 [5M]
b Explain the operation of Zener diode as a voltage regulator. L2 CO4 [5M]

UNIT-V

- 9 a Explain the working of a full-wave rectifier with the help of a circuit diagram and waveforms. L2 CO5 [5M]
b Explain Full adder circuit with the help of truth tables L2 CO5 [5M]

(OR)

- 10 a What is Excess-3 code? Encode the decimal numbers 0–9 using Excess-3 code. L3 CO5 [5M]
b Draw and explain the block diagram of a DC power supply. L2 CO5 [5M]
