



# ADITYA UNIVERSITY

B.Tech – I Semester End Examinations Supplementary – Mar 2026

## BASIC ELECTRICAL AND ELECTRONICS ENGINEERING (Common to CE, ME, ECE, CSE & Min.E)

**Time: 3 hours****Max. Marks: 100****Answer ONE question from each unit****All Questions Carry Equal Marks****All parts of the questions must be answered at one place only****UNIT-I**

- 1 a Explain kirchoffs laws with examples L2 CO1 [10M]  
b Define ohms law and write it's limitations L2 CO1 [10M]
- (OR)**
- 2 a Explain the following terms i) Cycle ii) Amplitude iii) Time period L2 CO1 [10M]  
iv) Frequency v) Instantaneous value vi) Peak to peak value  
b Explain the series and parallel connection of resistance with neat diagram L3 CO1 [10M]  
and derive the equivalent resistance

**UNIT-II**

- 3 a Explain the operation of DC motor with neat diagram. L2 CO2 [10M]  
b Explain the operation of transformer with neat diagram. L2 CO2 [10M]
- (OR)**
- 4 a Explain the working of Megger with neat diagram L2 CO2 [10M]  
b Explain the construction and working of repulsion type moving iron L2 CO2 [10M]  
instrument.

**UNIT-III**

- 5 a Explain the differences between conventional and non-conventional L2 CO3 [10M]  
energy resources.  
b Describe the layout and working principles of hydel power station L2 CO3 [10M]
- (OR)**
- 6 a Explain how electrical energy consumption is calculated for domestic L2 CO3 [10M]  
appliances.  
b Explain the causes and effects of electric shock and safety precautions L2 CO3 [10M]

**UNIT-IV**

- 7 a Explain the operation of zener diode and draw V-I characteristics with L2 CO4 [10M]  
neat circuit diagram.  
b Explain the operation of P-N junction diode and draw V-I characteristics. L2 CO4 [10M]
- (OR)**
- 8 a Explain common base mode of transistor & draw input, output L2 CO4 [10M]  
characteristics.  
b Compare the CB, CE, and CC configurations of a Bipolar Junction L1 CO4 [10M]  
Transistor

**(P.T.O)**

## UNIT-V

- 9 a Explain the operation of bridge rectifier & draw the wave forms & derive the expression for output voltage & current. L2 CO5 [10M]  
b Explain the types of filters used in rectifier circuits L2 CO5 [10M]
- (OR)**
- 10 a Explain the basic logic gates with truth table L2 CO5 [10M]  
b Explain the concept and importance of coding systems such as BCD, Excess-3, Gray code, and Hamming code. L2 CO5 [10M]

\*\*\*\*\*